

Analog Circuits


Operational Amplifiers (Opamps)

DC Power Supplies

Oscillators

Operational Amplifiers

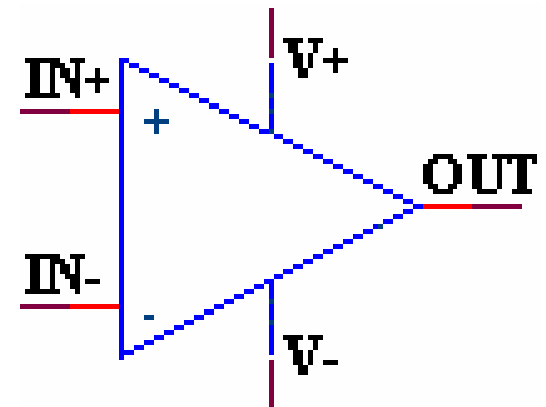- High-gain differential amplifier, using voltage feedback, providing stabilized voltage gain
- Symbol of differential amplifier
 - inputs
 - Inverting input (IN-)
 - Non-inverting input (IN+)
 - output (OUT)
 - dc power supplies
 - Positive supply (V+)
 - Negative supply (V-)




Characteristics

- Very high input impedance (ideal ∞ - infinite input resistance)
- Very small input currents (ideal 0)
- Very high amplification (voltage gain) (A_v -ideal ∞)
- Output voltage bounded by power supplies values
- Very small difference between the absolute values of input voltages (ideal 0)
- Very small output impedance (ideal 0 – zero output resistance)
- Two operation modes:
 - differential mode: $V_d = V_{IN+} - V_{IN-}$
 - common mode: $V_c = (V_{IN+} + V_{IN-})/2$

(useful mode for rejecting noise signals);


common mode rejection ratio CMRR parameter defined; expressed logarithmically in decibels dB:
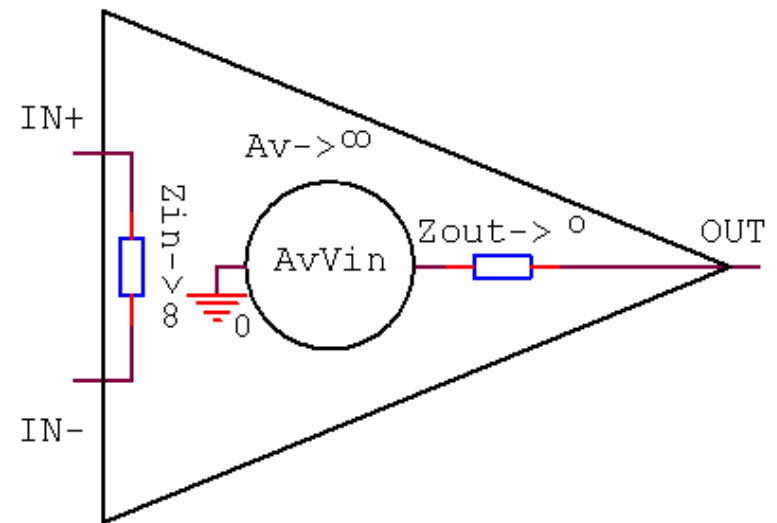
$$\text{CMRR[dB]} = 20\log_{10}(A_d/A_c)$$



Negative Reaction (feedback)

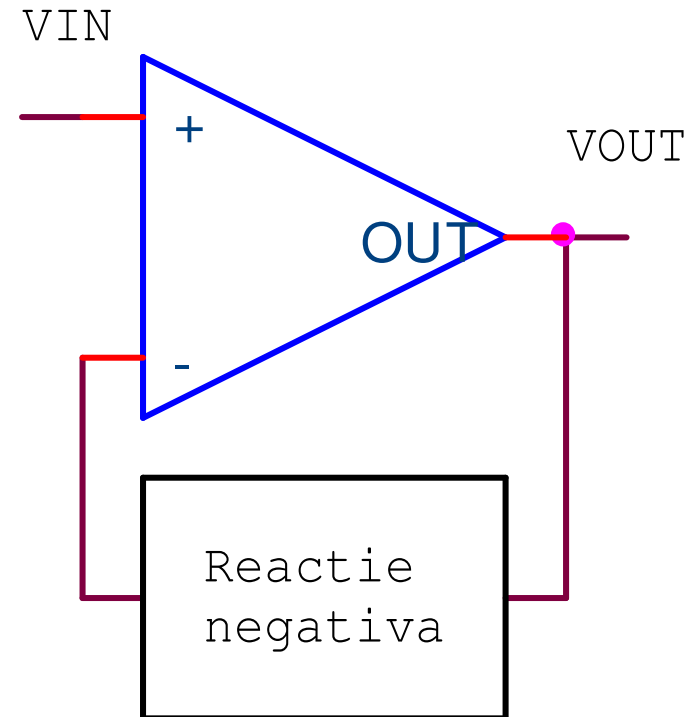- An amount of the output signal is fed back to circuit's input, with a phase shift of 180° from input signal, implying a decrease of the output signal







Constant-Gain OpAmp

- $V_1 = 0V$
- $I_{R1} = I_{R2}$

$$I = \frac{V_{IN}}{R_1} = -\frac{V_{OUT}}{R_2}$$

$$V_{OUT} = -\frac{R_2}{R_1} V_{IN}$$

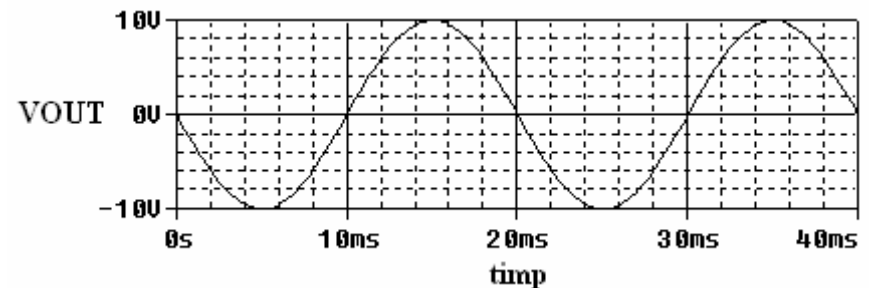
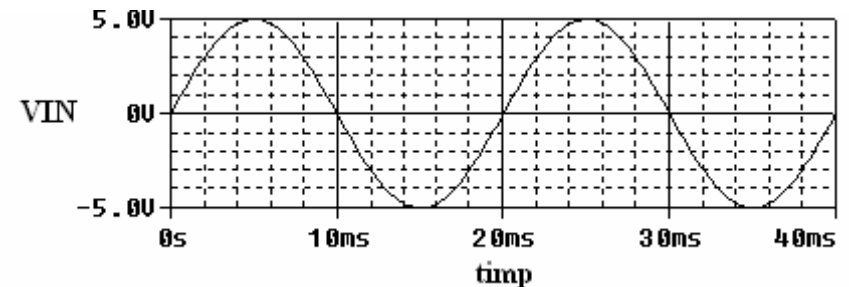
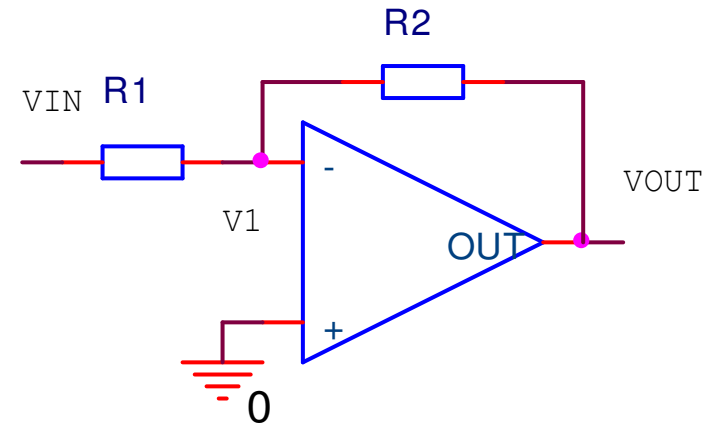
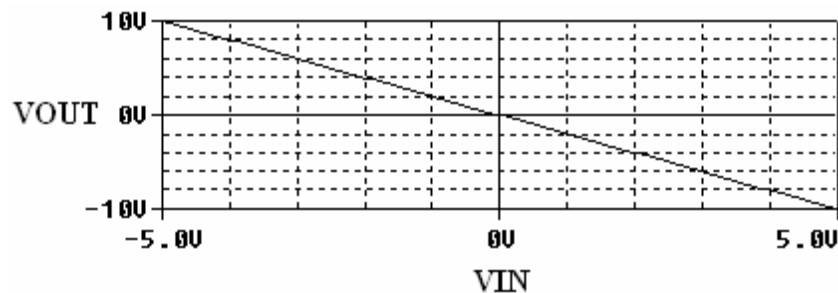


Noninverting OpAmp

- $V_{IN} = V_1$
- $I_{R1} = I_{R2}$

$$V_{IN} = V_1 = \frac{R_1}{R_1 + R_2} V_{OUT}$$
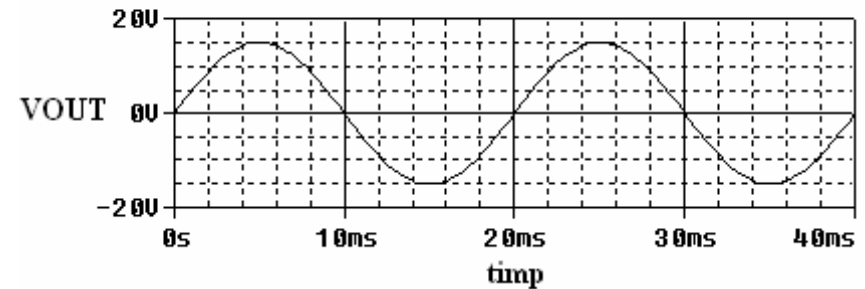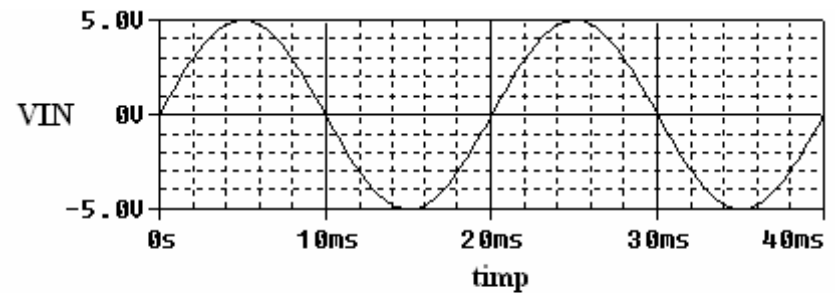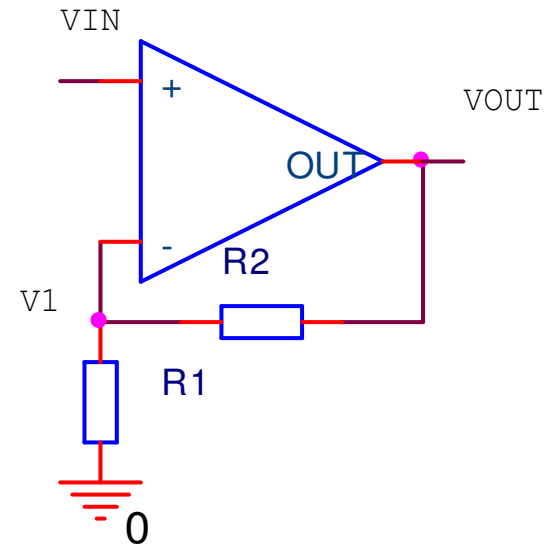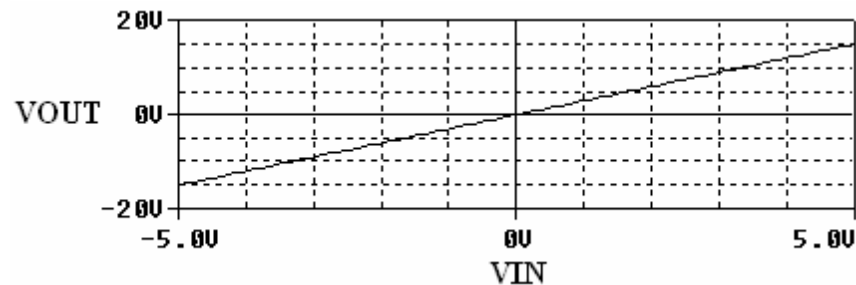
$$V_{OUT} = \left(1 + \frac{R_2}{R_1}\right) V_{IN}$$






Summing OpAmp

- $V_1 = 0V$
- $I_{R2} = I_{R11} + \dots + I_{R1n}$

$$I_{R2} = -\frac{V_{OUT}}{R_2} = \frac{V_{IN1}}{R_{11}} + \dots + \frac{V_{INn}}{R_{1n}}$$
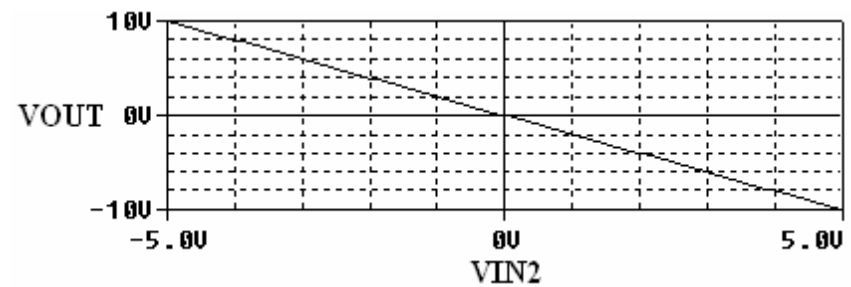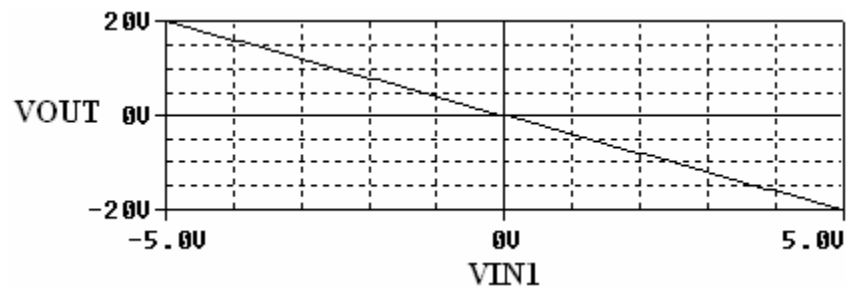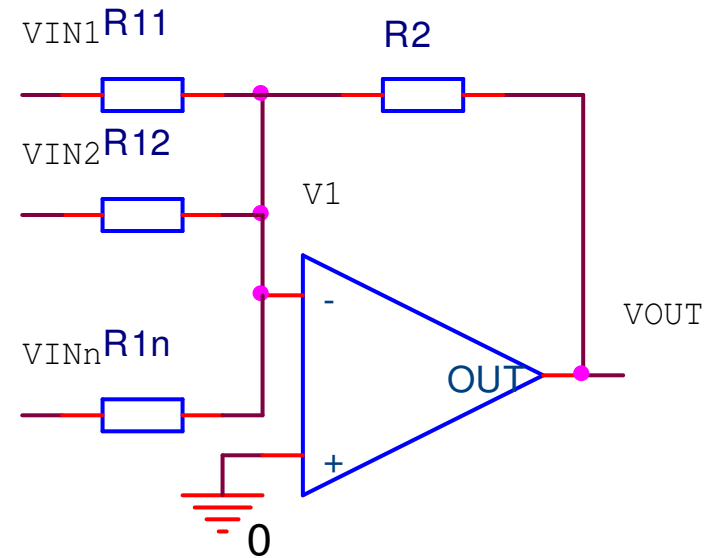
$$V_{OUT} = -\left(\frac{R_2}{R_{11}}V_{IN1} + \dots + \frac{R_2}{R_{1n}}V_{INn}\right)$$






Integrator

$$Z_c = \frac{1}{j\omega C} = \frac{1}{sC}$$

- $V_1 = 0V$
- $I_R = I_C$

$$I = \frac{V_{IN}}{R_1} = -\frac{V_{OUT}}{Z_C} = -sCV_{OUT}$$

$$V_{OUT} = -\frac{1}{sCR} V_{IN}$$

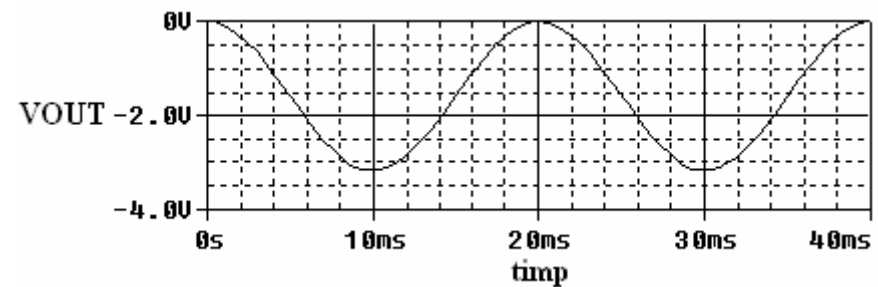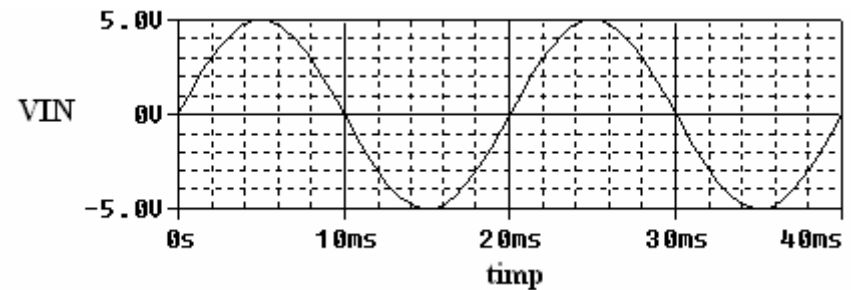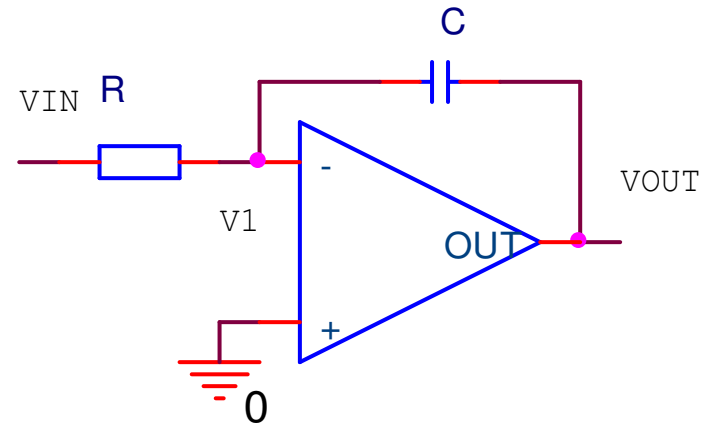




Differentiator

$$Z_c = \frac{1}{j\omega C} = \frac{1}{sC}$$

- $V_1 = 0V$
- $I_R = I_C$

$$I = -\frac{V_{OUT}}{R} = \frac{V_{IN}}{Z_c} = sCV_{IN}$$

$$V_{OUT} = -sCRV_{IN}$$

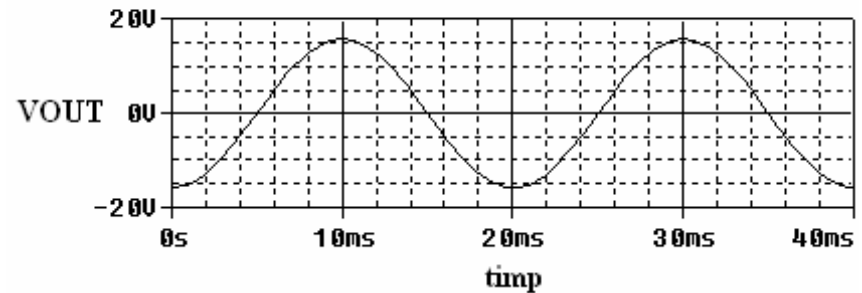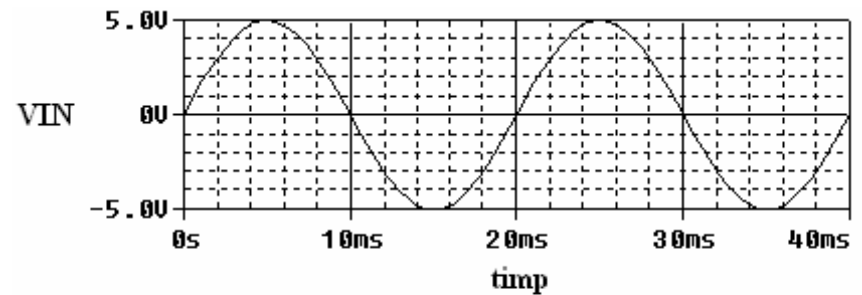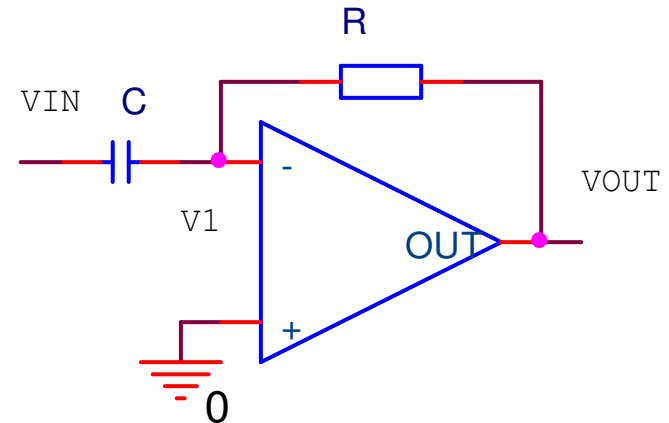

Power Supply Circuits



Convert analog supply voltage into desired regulated dc voltage

Circuit consists on:

- transformer: separates circuit from ac power supply network and steps input ac voltage to a desired ac level, conform to the needed dc voltage level to be obtained
- rectifier: to half-wave or full-wave rectify the ac signal, getting a dc component non zero
- filter: attenuation of ac voltage irregularities (as coming from rectifier)
- voltage regulator: regulates the filtered dc voltage to a desired value for output voltage

Half-Wave Rectifier

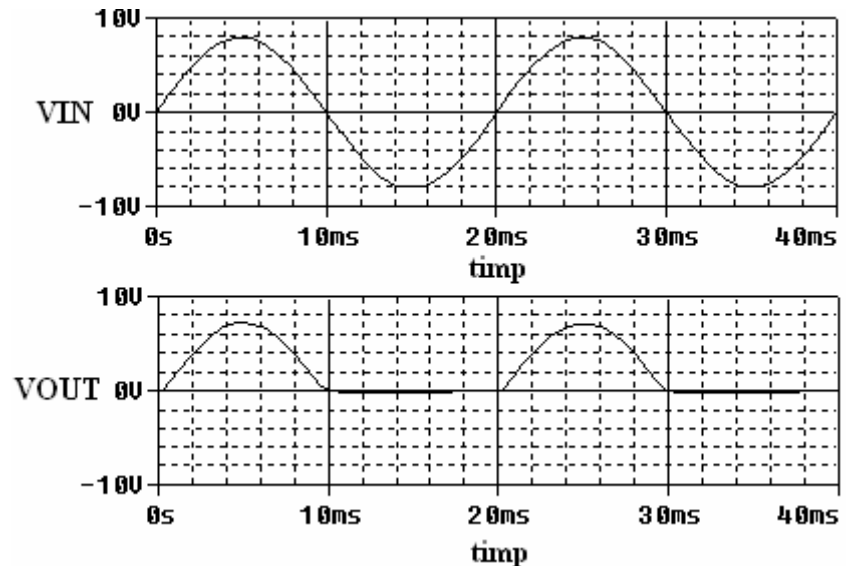
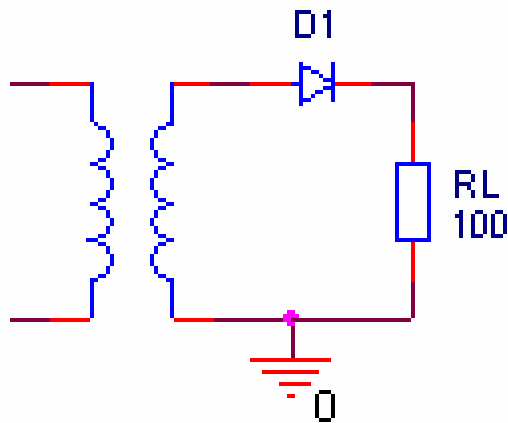
- D_1 is open for positive polarities and off for negative polarities of the applied input voltage



Full-Wave Bridge Rectifier

Four diodes in a bridge configuration

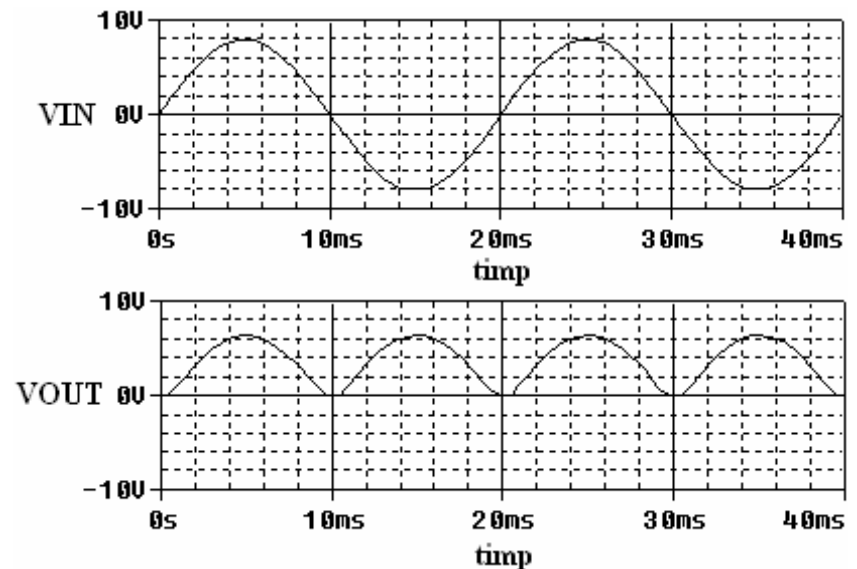
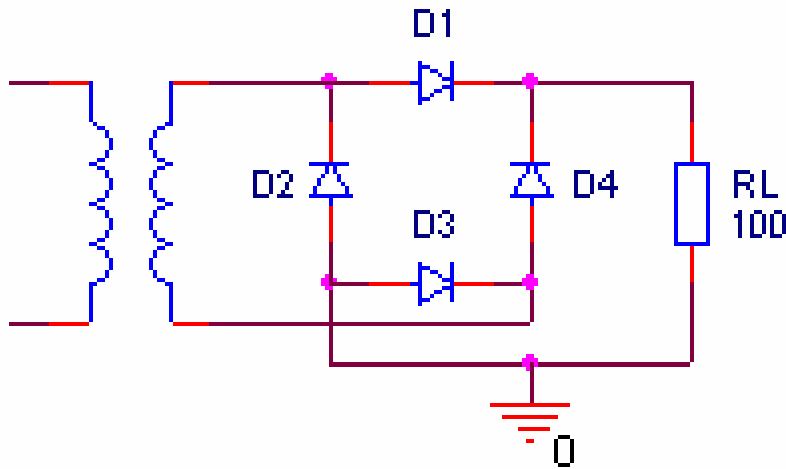
- D_1 and D_3 are open for positive waves
- D_2 and D_4 are open for negative waves of applied input voltage



Rectifier with filtered output

A capacitor C_1 in parallel with load resistance R_L

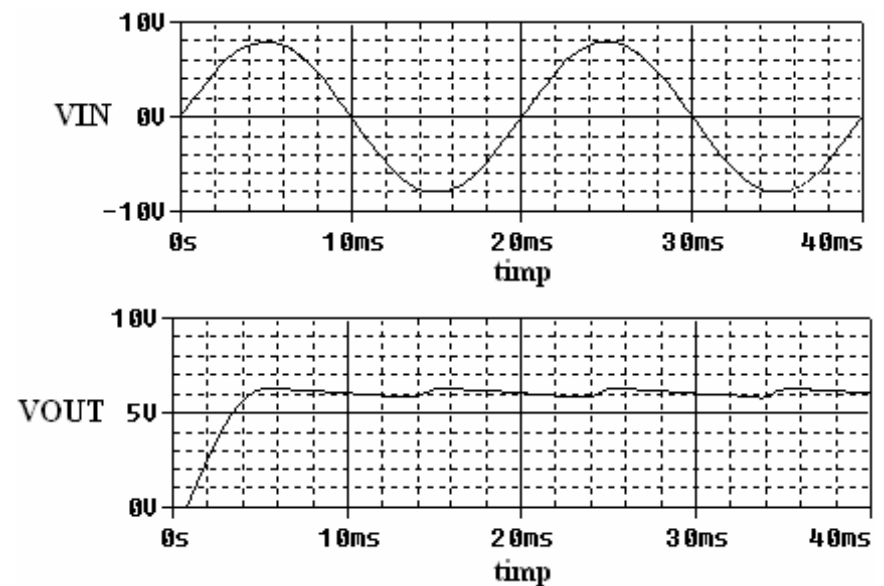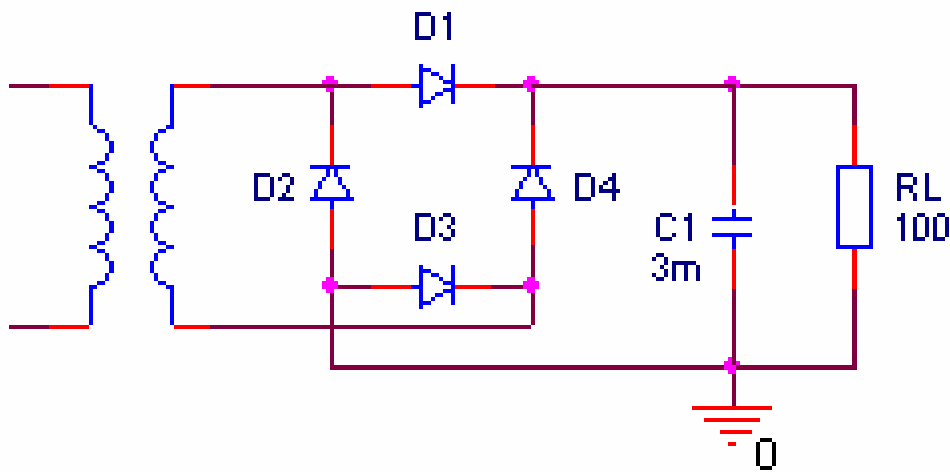- If rectifier provides a higher voltage than the voltage drop on capacitance, it stores energy
- If rectifier provides a lower voltage than capacitor's voltage drop, C_1 will generate energy





Voltage Regulators

Zener diode shunt regulator

Output voltage must stay fixed, for different loads (R_L values)



Filtered output voltage has a dc component and some ac variations (ripple voltage)

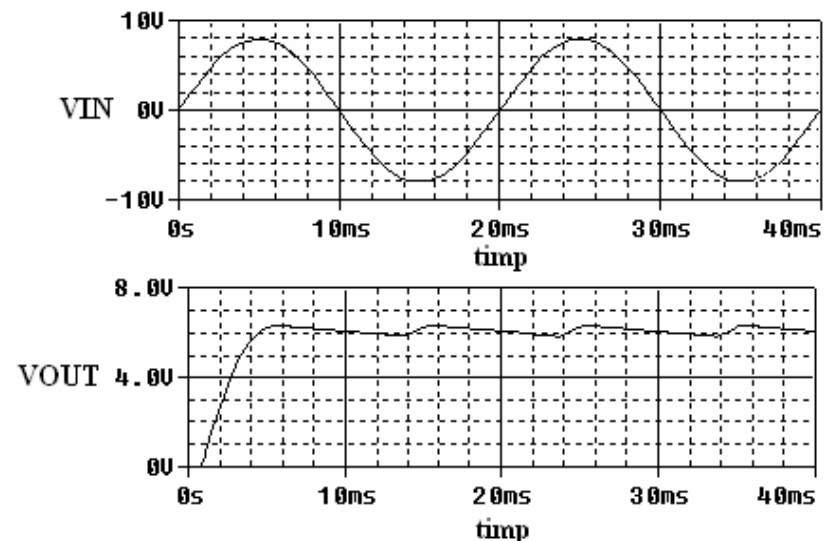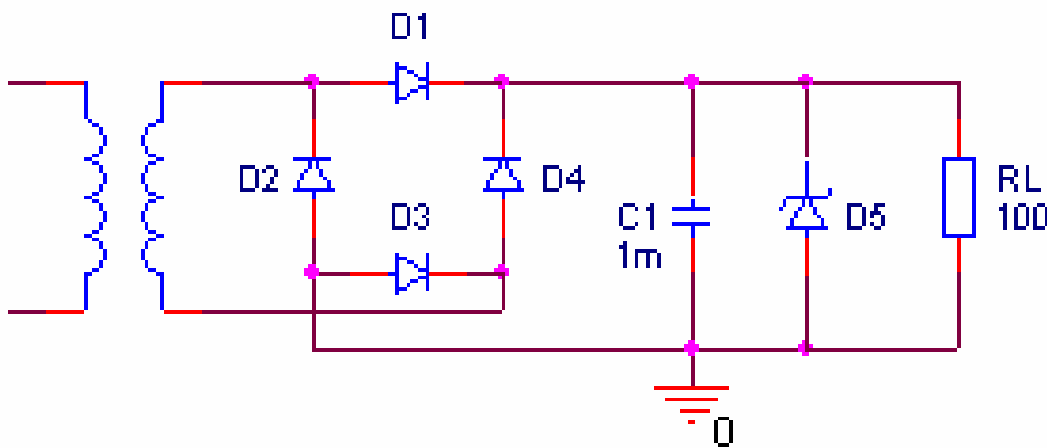- Zener diode shunt regulator based on non-linearity of the current-voltage characteristics for a Zener diode
- Allows for high variations of output currents, for small variations of diode's reverse voltage drop



Voltage regulator with negative feedback and without error amplifier

- Negative feedback from collector to base circuit of Q1
- Output voltage (v_{OUT}) compared with a reference voltage (v_Z)
- comparison generates an error signal applied to a control element
- if v_{OUT} increases, control element (negative reaction) will impose voltage decrease, and vice-versa
- For transistor Q1: $v_{BE} = v_Z - v_{OUT}$
- if v_{OUT} goes higher $\rightarrow v_{BE}$ lower $\rightarrow v_{CE}$ higher $\rightarrow v_{OUT}$ lower
- if v_{OUT} lower $\rightarrow v_{BE}$ higher $\rightarrow v_{CE}$ lower $\rightarrow v_{OUT}$ higher
- $V_{OUT} = V_Z - V_{BE}$

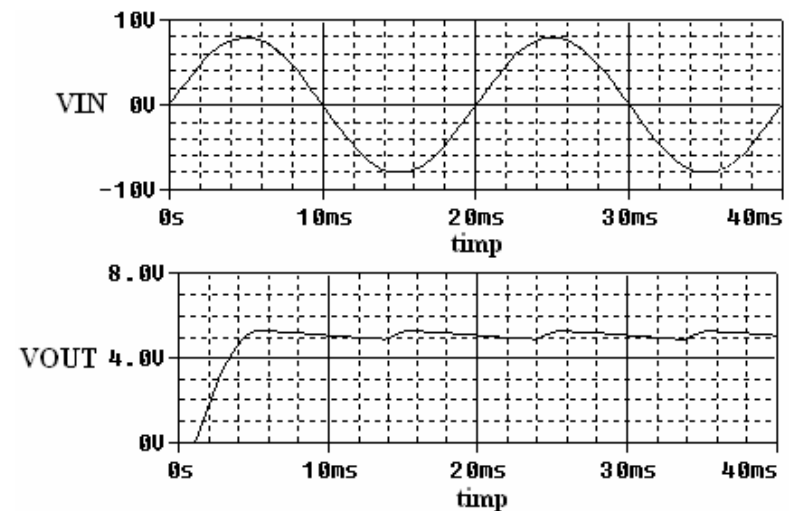
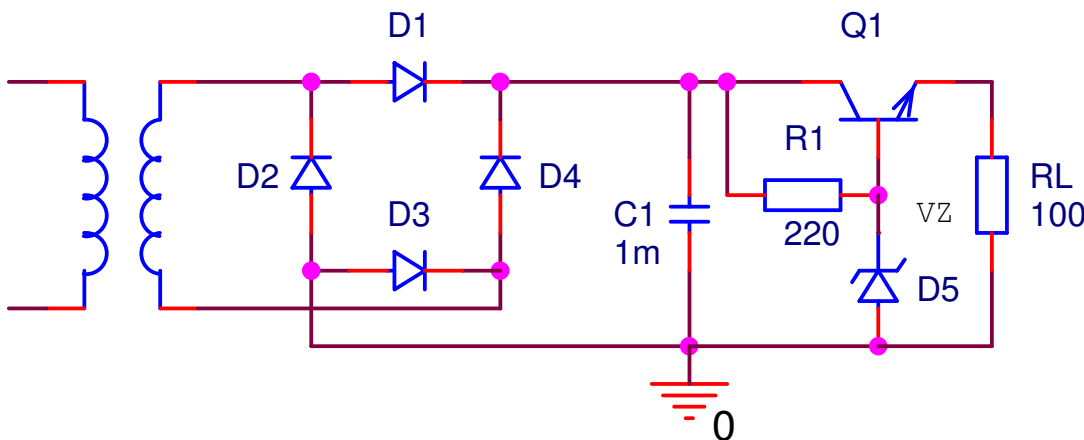


Voltage regulator with feedback and error amplifier

$$v_1 = \frac{R_3}{R_2 + R_3} v_{OUT}$$


- if v_{OUT} lower $\rightarrow v_1$ lower $\rightarrow v_2$ higher $\rightarrow v_{BE}$ higher $\rightarrow v_{CE}$ lower $\rightarrow v_{OUT}$ higher
- if v_{OUT} higher $\rightarrow v_1$ higher $\rightarrow v_2$ lower $\rightarrow v_{BE}$ lower $\rightarrow v_{CE}$ higher $\rightarrow v_{OUT}$ lower
- Because $v_1 = v_Z$
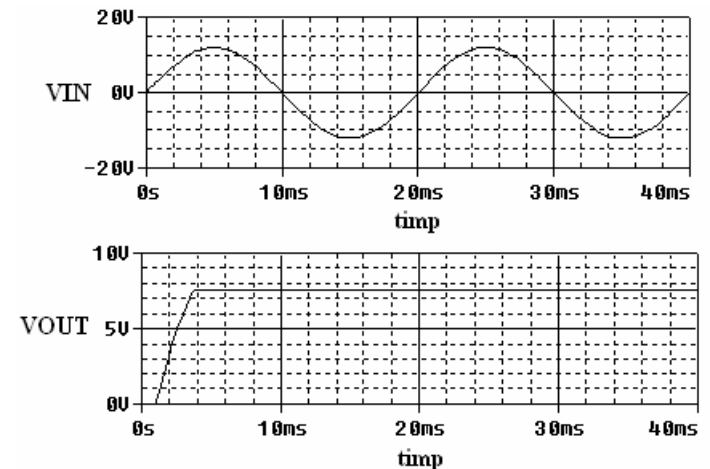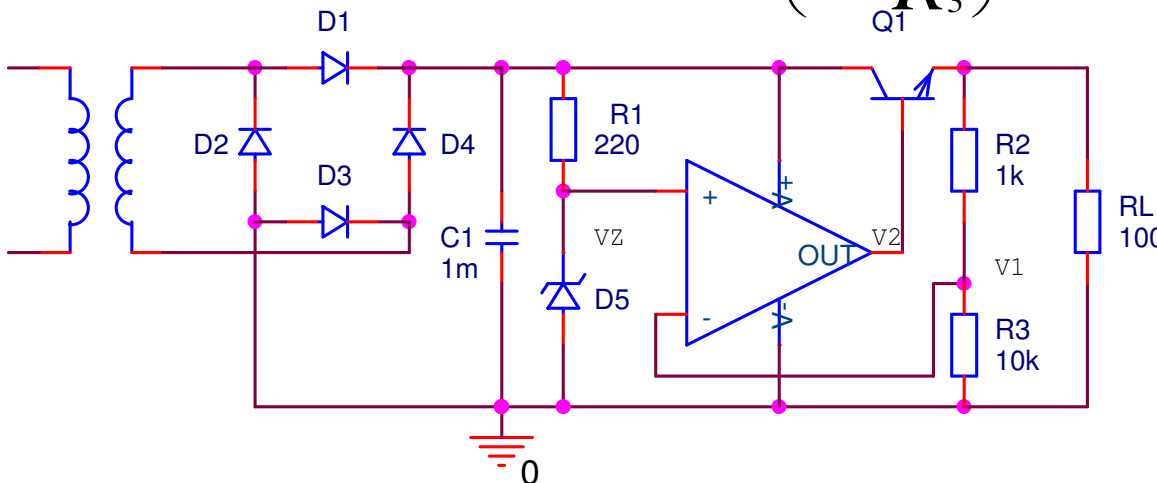
$$v_{OUT} = \left(1 + \frac{R_2}{R_3} \right) v_Z$$




Integrated Circuits (IC Regulators)

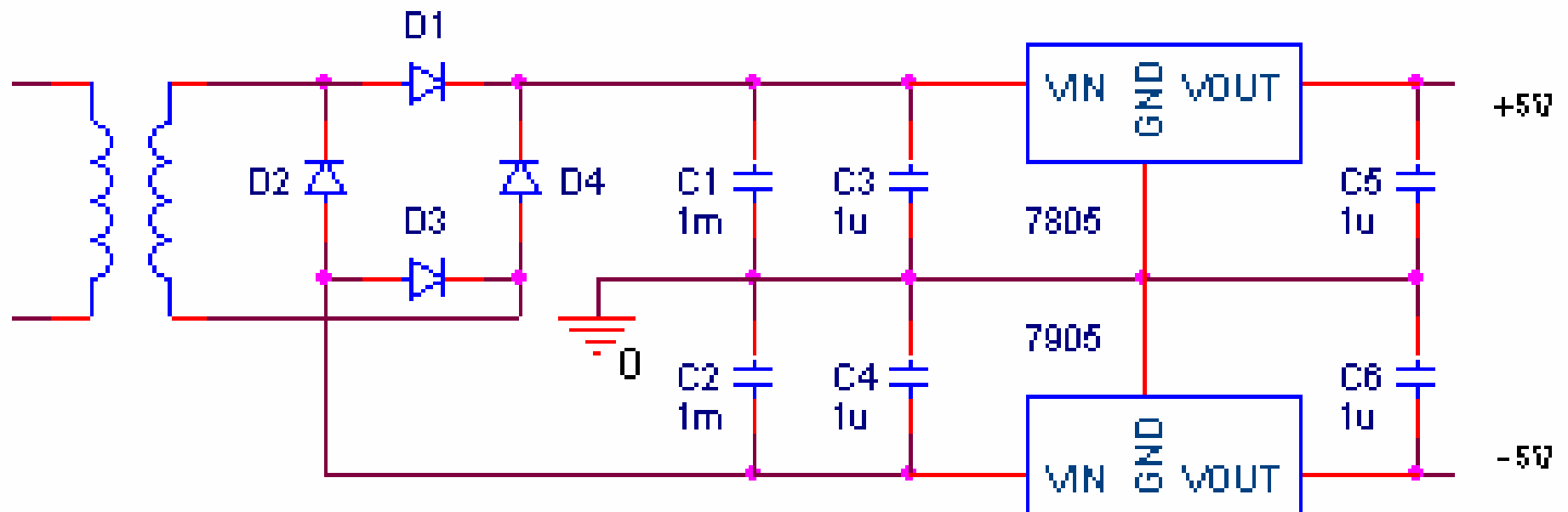- 7800 series provides positive output regulated voltages
- 7900 series provides negative output regulated voltages
- Last two digits from code show regulated voltage value
- Input capacitance avoids oscillations due to stray inductances of supply line
- Output capacitance acts as filter



Oscillators

- Generates a repetitive waveform, without any input stimulus
- Amplifier and positive feedback
- Positive feedback: an amount of output voltage is fed back to input with zero phase shift, providing a gain of the output voltage
- Conditions for having oscillations:
 - Total phase shift must be zero
 - Voltage gain must be greater than 1 for obtaining desired oscillations amplitude. After gaining desired amplitude for oscillations, voltage amplification must stay at 1

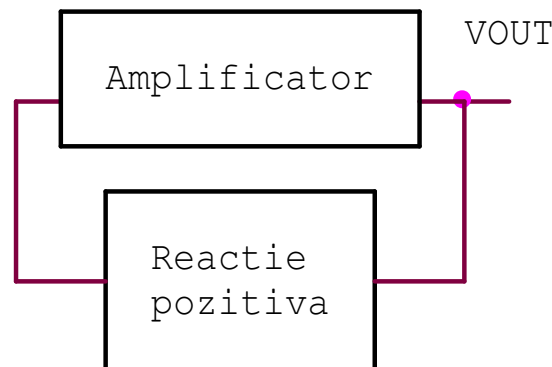

Wien bridge Oscillator


- Positive feedback circuit, made up by an op-amp and RC bridge circuit

Wien bridge

- RC high-pass and RC low-pass filters
- Each filter operates over 'edge' frequencies (frequency adjustment)
- $R_1=R_2=R$, $C_1=C_2=C$
- attenuation is minimum for oscillation frequency

$$f_{osc} = \frac{1}{2\pi RC}$$

$$\frac{V_{IN}}{V_{OUT}} = 3$$

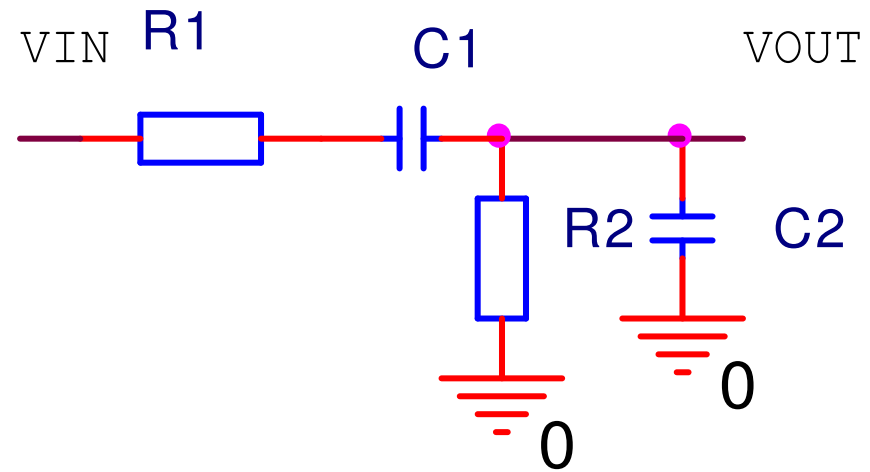

- Base circuit



- Op-amp with negative feedback
- For having a unit voltage gain for oscillator, amplification for base circuit must be 3



$$\frac{V_{OUT}}{V_{IN}} = 1 + \frac{R_2}{R_1} \quad R_2 = 2 R_1$$

- For lower oscillation amplitudes the two Zener diodes are off (no direct diode current)

$$\frac{V_{OUT}}{V_{IN}} = 1 + \frac{R_2 + R_3}{R_1} = 3 + \frac{R_3}{R_1}$$

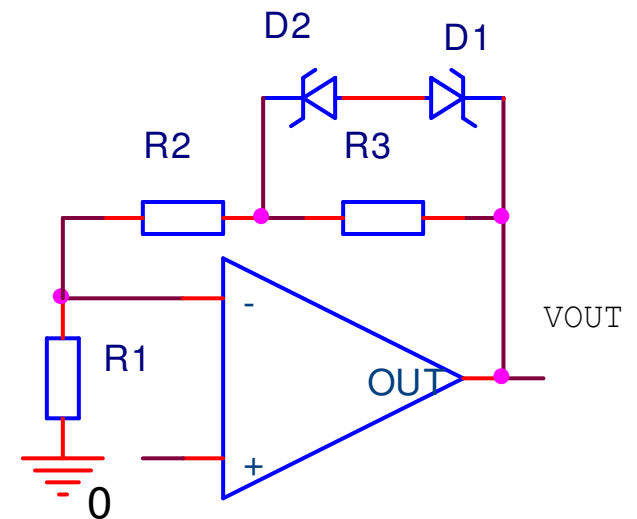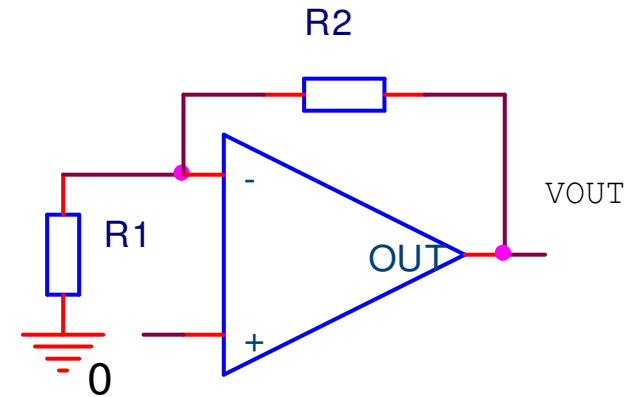- When having desired amplitude, the diodes go conducting, shorting R3 and giving a voltage gain for the base circuit of 3, and a voltage gain for oscillator of 1



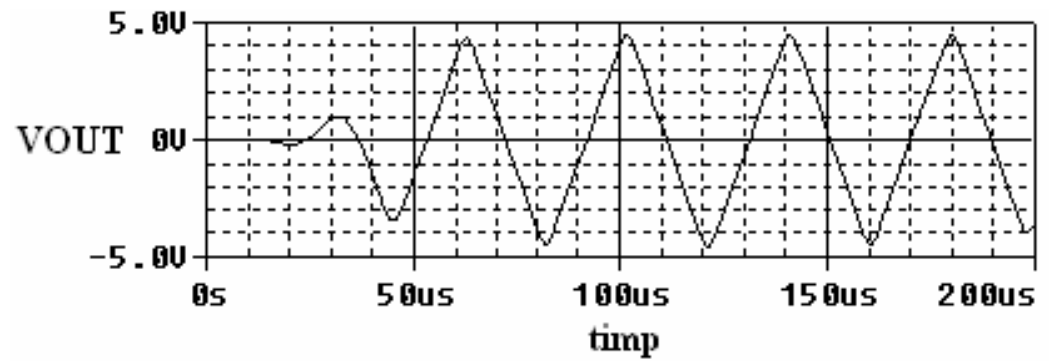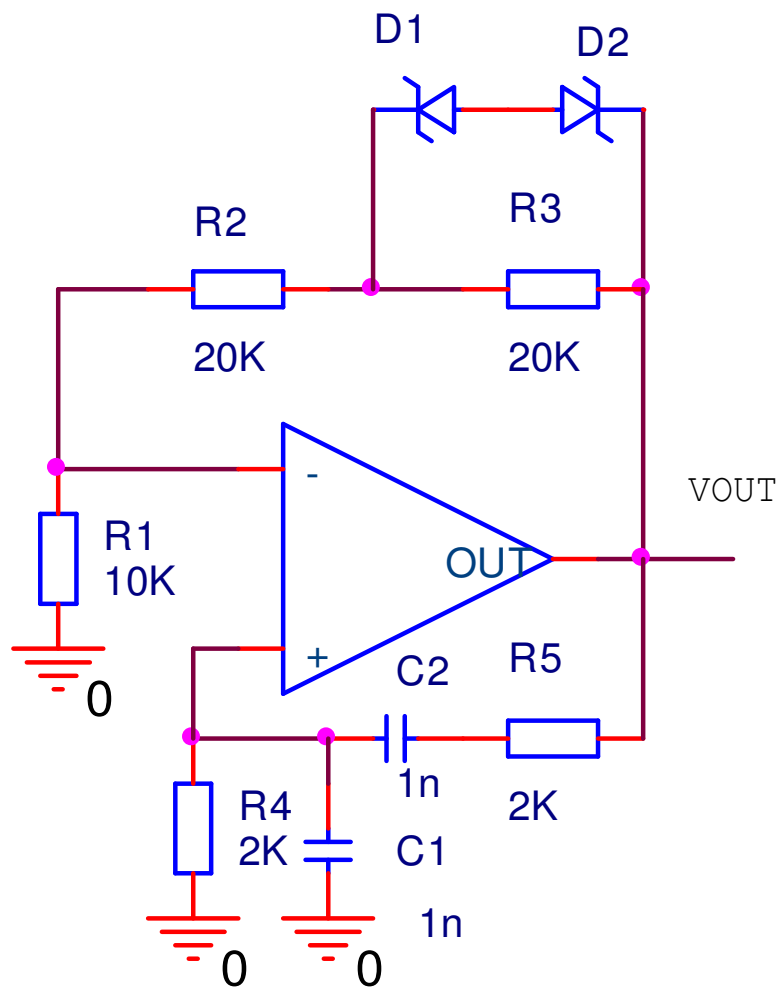

Wien bridge oscillator

Problem

Design a current source, being voltage driven

- AO2 – repeater
- For calculus of V_- superposition paradigm is used

$$V_- = \frac{R_2}{R_1 + R_2} V_1 + \frac{R_1}{R_1 + R_2} V_2$$


$$V_+ = \frac{R_3}{R_3 + R_4} V_3$$

$$V_- = V_+$$

$$\frac{R_2}{R_1 + R_2} V_1 + \frac{R_1}{R_1 + R_2} V_2 = \frac{R_3}{R_3 + R_4} V_3$$

$$I_s = I_5 = \frac{V_2 - V_3}{R_5}$$

$$V_2 = I_s R_5 + V_3$$

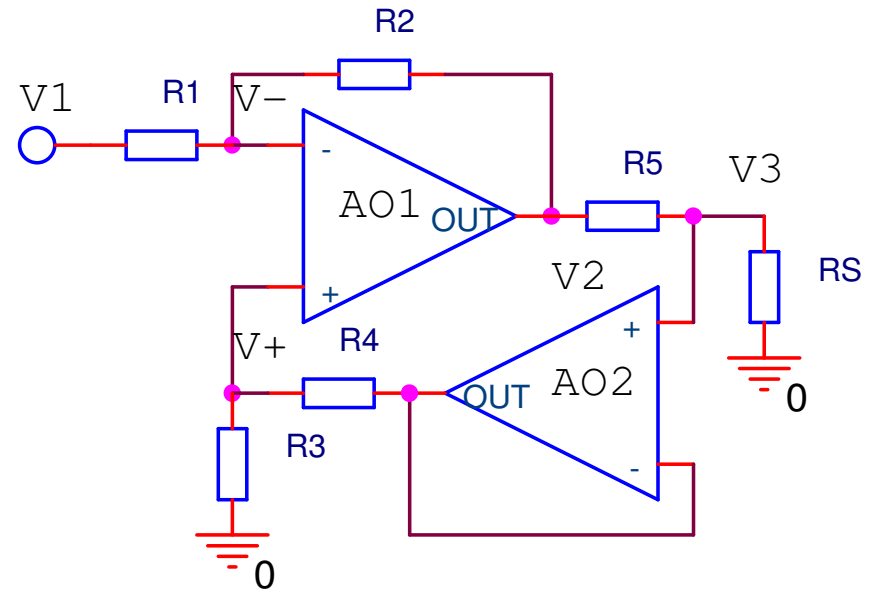

$$\frac{R_2}{R_1 + R_2} V_1 = \frac{R_3}{R_3 + R_4} V_3 - \frac{R_1}{R_1 + R_2} (I_s R_5 + V_3)$$

$$I_s = -\frac{R_2}{R_5 R_1} V_1 + \frac{R_1 + R_2}{R_5 R_1} \left(\frac{R_3}{R_3 + R_4} - \frac{R_1}{R_1 + R_2} \right) V_3$$

- I_s must depend only on V_1
- V_3 coefficient must be 0

$$\frac{R_1 + R_2}{R_5 R_1} \left(\frac{R_3}{R_3 + R_4} - \frac{R_1}{R_1 + R_2} \right) = 0$$

$$R_2 R_3 = R_1 R_4$$

$$I_s = -\frac{R_2}{R_5 R_1} V_1$$

