

2017_1_A1

Design a 32-bit ALU for the following operations: ADD, SUB, INC, DEC, SLT. Design the 1-bit ALU by using only one adder and the minimum number of components and control signals. Extend the 1-bit ALU to obtain the 32-bit ALU. Show the schematic with control signals and a table with the control signal values for the required operations.

ADD $\rightarrow a + b \rightarrow C_IN = 0$


SUB $\rightarrow a - b \rightarrow a + \text{NOT}(b) + 1 \rightarrow C_IN = 1$

INC $\rightarrow a - 1 \rightarrow a + 0 + 1 \rightarrow C_IN = 1$

DEC $\rightarrow a - 1 \rightarrow a + \text{NOT}(1) + 1 \rightarrow C_IN = 0$

NOT(0) \rightarrow extended on 32 bits only $\rightarrow 0xFFFFFFFF$

 $0x78 - 0x01$
 $0b0111\ 1000 - 0b0000\ 0001$
 $0b0111\ 1000 + 0b1111\ 1110 + 0b0000\ 0001$
 $\rightarrow 0b0111\ 1000 + 0b1111\ 1111$
 $0b0111\ 0111 \rightarrow 0x77$



1-bit ALU (for 32-bit ALU see lecture 5, cascade 32 times, MSB result from adder of ALU_31 connected to Less input of ALU_0, rest of Less signals connected to 0)

Operation	B_Negat	C_in	Op
ADD	00	0	0
SUB	01	1	0
INC	10	1	0
DEC	11	0	0
SLT	01	1	1

2017_2_A1: ADD, SUB, INC, DEC, SLT, AND, OR, NAND, NOR.

NAND \rightarrow De Morgan $\rightarrow \text{NOT}(A) \text{ OR } \text{NOT}(B)$

NOR \rightarrow De Morgan $\rightarrow \text{NOT}(A) \text{ AND } \text{NOT}(B)$

2017_1_B1

Design a 16-bit ALU for ADD, SUB, INC and DEC, for 16-bit operands or 2 x 8-bit operands (MMX style). Draw the schematic with control signals using two 8-bit adders and the necessary auxiliary circuits. Show a table with the values of the control signals for the required operations.


ADD $\rightarrow a + b \rightarrow C_IN = 0$

SUB $\rightarrow a - b \rightarrow a + \text{NOT}(b) + 1 \rightarrow C_IN = 1$

INC $\rightarrow a - 1 \rightarrow a + 0x00 + 1 \rightarrow C_IN = 1$

DEC $\rightarrow a - 1 \rightarrow a + 0xFF + 0 \rightarrow C_IN = 0$

Operation	B_Negat	C_in_0	C_in_1	Sel
ADD – 2x8-bits	00	0	0	1
SUB – 2x8-bits	01	1	1	1
INC – 2x8-bits	10	1	1	1
DEC – 2x8-bits	11	0	0	1
ADD – 16 bits	00	0	X	0
SUB – 16 bits	01	1	X	0
INC – 16 bits	10	1	X	0
DEC – 16 bits	11	0	X	0

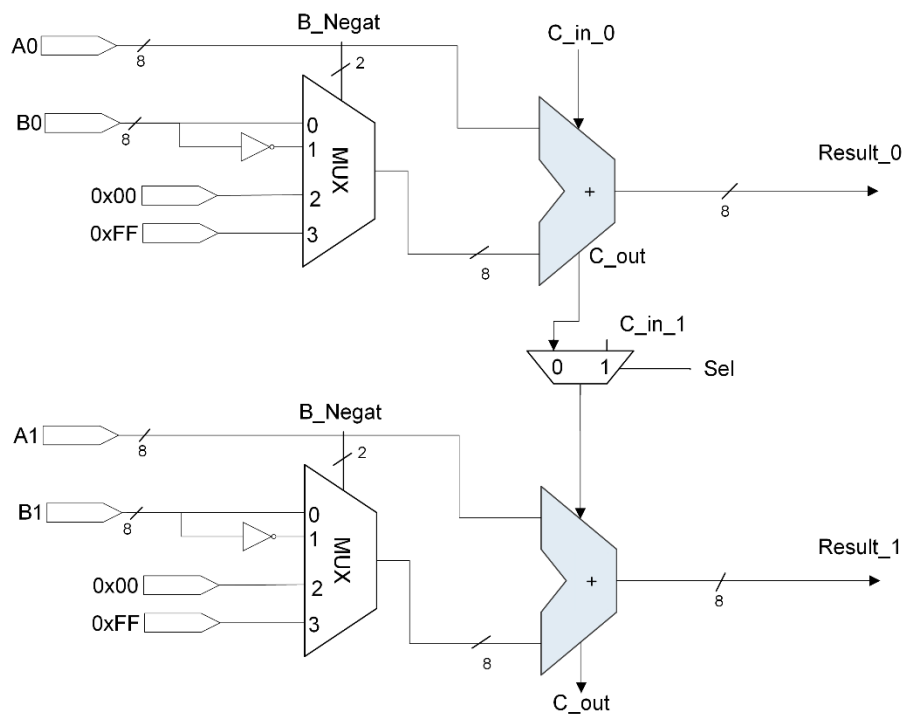

Problems: Add instructions in Single-Cycle MIPS.

BLTZ (branch on less than zero) → I-type instruction

bltz rs, imm

RTL abstract:

If (RF[rs] < 0) then $PC \leftarrow PC + 4 + \text{Sign_Ext}(\text{Imm} \ll 2)$;

Else $PC \leftarrow PC + 4$

Added a control signal specific for BLTZ instruction. In order to differentiate from other branch instructions we add an OR gate before the PCSrc control signal. The OR gate inputs are the normal branch decision and the new bltz decision.

BNE (branch on not equal) → I-type instruction

bne rs, rt, imm

RTL abstract:

If (RF[rs] != RF[rt]) then $PC \leftarrow PC + 4 + \text{Sign_Ext}(\text{Imm} \ll 2)$;

Else $PC \leftarrow PC + 4$


ADDM (add memory: adds the content of a register to a memory location and writes the result in the Register File) → I-type instruction

RTL abstract:

addm rs, rt, imm

$RF[rt] \leftarrow M[RF[rs] + \text{Sign_Ext}(\text{Imm})] + RF[rt]$; $PC \leftarrow PC + 4$;

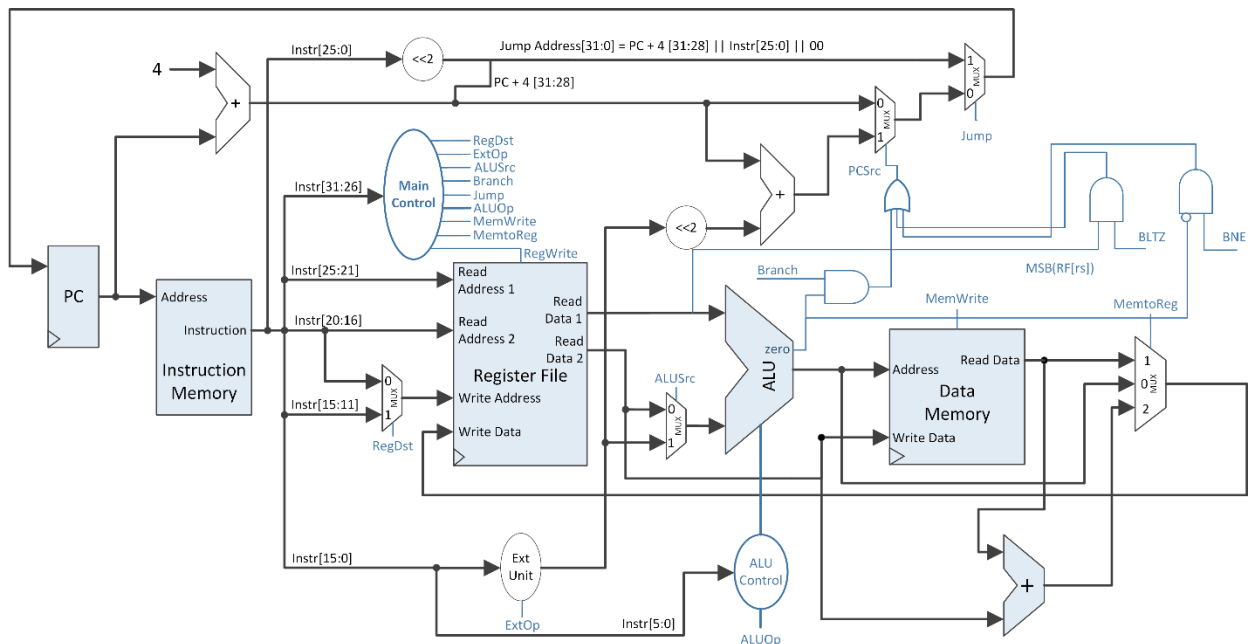- Added a 32-bit adder for the computation
- Extended the MemToReg MUX to 3-inputs.



Single-cycle data-path extended for BLTZ, BNE, ADDM

Instruction	Reg Dst	Reg Write	Ext Op	ALU Src	ALU Op	Mem Write	Memto Reg	Branch	BNE	BLTZ	JUMP
bltz	X	0	1	X	XX	0	XX	0	0	1	0
bne	X	0	1	0	01 (-)	0	XX	0	1	0	0
addm	0	1	1	1	00 (+)	0	10	0	0	0	0

Usually we treat X (don't care) as 0.

Problems: Add instructions in Single-Cycle MIPS:

JAL (jump and link) instruction and JR (jump register).


JAL RTL abstract

Single cycle: $PC \leftarrow PC[31:28] || \text{target_address} || 00$; $RF[31] \leftarrow PC + 4$;

Pipeline: $PC \leftarrow PC[31:28] || \text{target_address} || 00$; $RF[31] \leftarrow PC + 8$; (1 instruction will enter in the pipeline until the jump target address is known)


JR RTL abstract

Single cycle: $PC \leftarrow RF[rs]$;

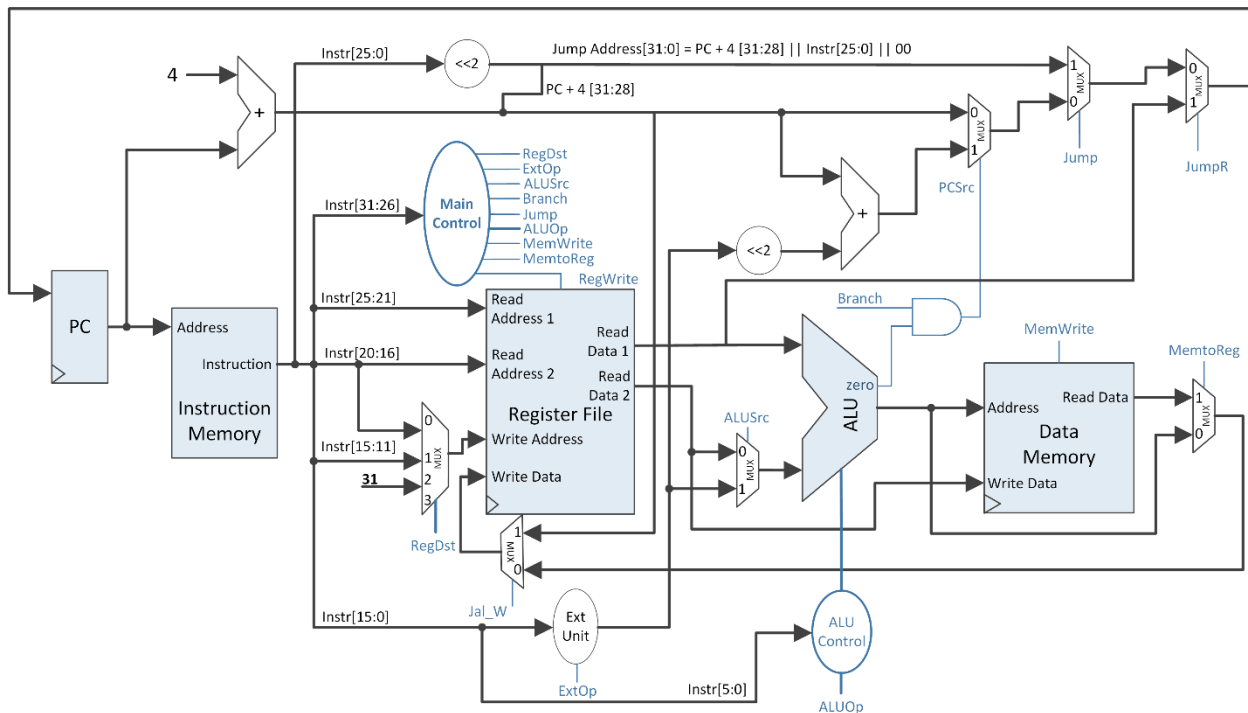

Single cycle data-path extended for JAL and JR instructions

Instruction	Reg Dst	Reg Write	Ext Op	ALU Src	ALU Op	Mem Write	Memto Reg	Branch	JUMP	Jal_W	JumpR
Jal	10	1	X	X	XX	0	X	0	1	1	0
jr	XX	0	X	X	XX	0	X	0	0	X	1

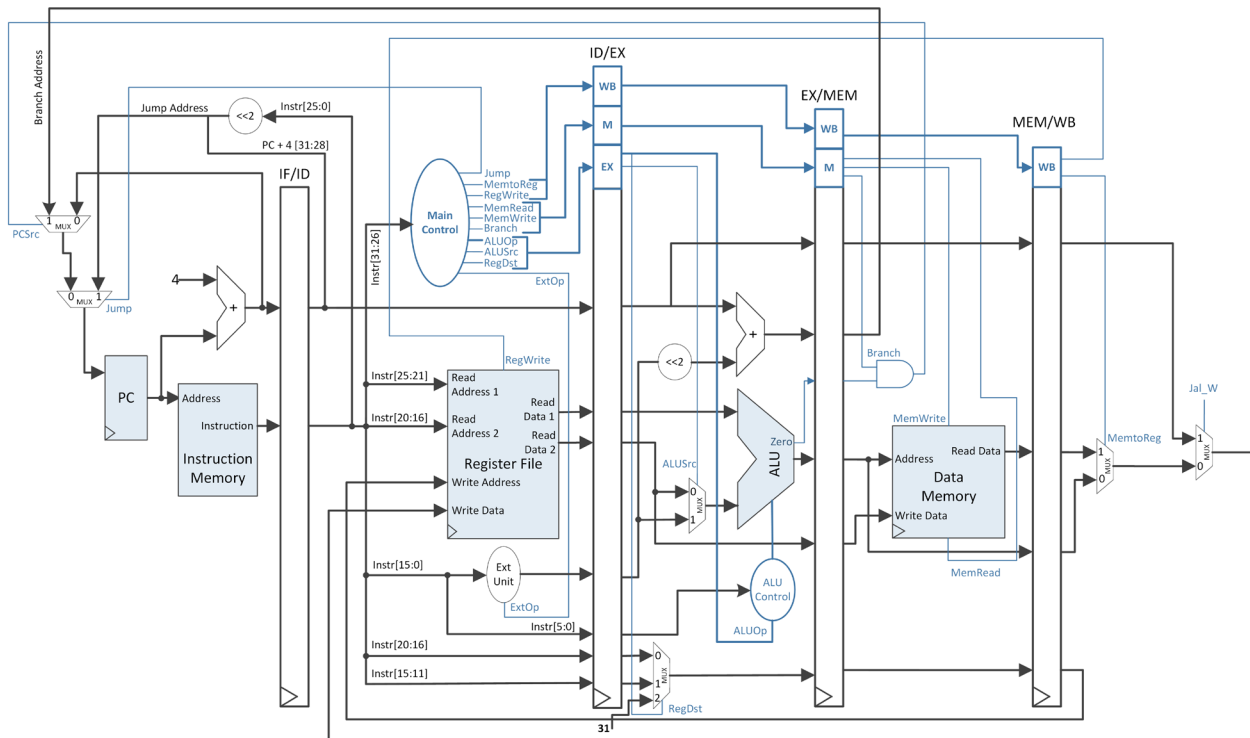

Pipeline data-path extended with JAL instruction

Cache memory problems

A 32-bit CPU generates 32-bit addresses for a byte addressable memory. Design a **256KB** cache memory for this CPU. The block size is 64 bytes. Show the block diagram, and the address decoding for a direct mapped cache memory and a 4-way set associative cache memory.

Direct Mapped

$$256 \text{ KB} = 2^8 \times 2^{10} \text{ B} = 2^{18} \text{ B}$$

$$\text{Block size} = 64 \text{ bytes} = 2^6 \text{ bytes}$$

$$\text{Data 32-bits} = 4 \text{ B} = 2^2 \text{ bytes}$$

$$\text{No of blocks} = 256 \text{ KB} / 64 \text{ B} = 2^{18} / 2^6 = 2^{12} \text{ blocks}$$

$$\text{Block offset} = 2^6 / 2^2 = 2^4$$

$$\text{Tag: } 32 - 12 - 4 - 2$$

→ 18 bits address

→ 6 bits address

→ 2 bits – byte offset

→ 12 bits – block index

→ 4 bits – block offset

→ 14 bits – tag

4-way set associative cache

$$256 \text{ KB} = 2^8 \times 2^{10} \text{ B} = 2^{18} \text{ B}$$

$$\text{Block size} = 64 \text{ bytes} = 2^6 \text{ bytes}$$

$$\text{Data 32-bits} = 4 \text{ B} = 2^2 \text{ bytes}$$

$$\text{No. of sets} = 4 \rightarrow 256 \text{ KB} / 4 = 64 \text{ KB}$$

$$\text{No of blocks} = 64 \text{ KB} / 64 \text{ B} = 2^{16} / 2^6 = 2^{10} \text{ blocks}$$

$$\text{Block offset} = 2^6 / 2^2 = 2^4$$

$$\text{Tag: } 32 - 10 - 4 - 2$$

→ 18 bits address


→ 6 bits address

→ 2 bits – byte offset


→ 10 bits – block index

→ 4 bits – block offset

→ 16 bits – tag

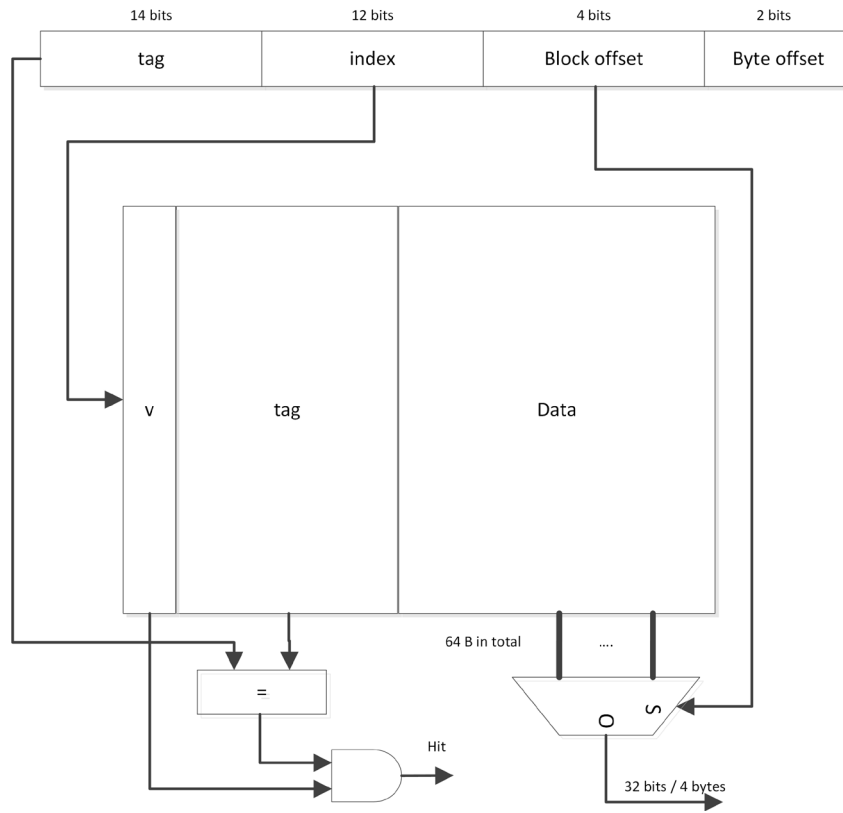

Direct mapped cache

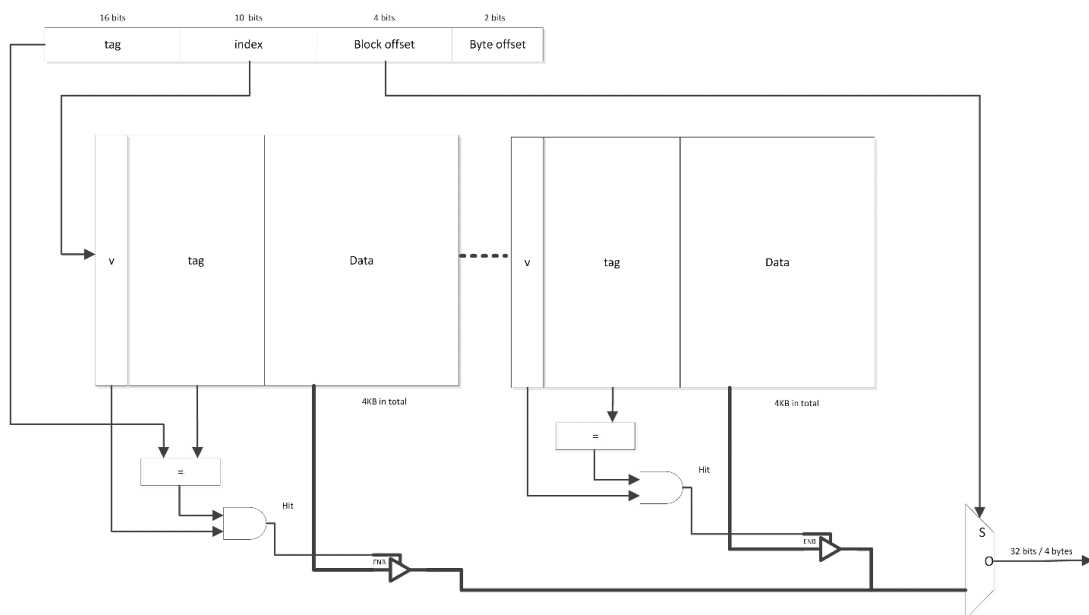

4-way set associative cache

Pipeline diagrams:

Draw the pipeline diagram with and without forwarding for the following code sequence: lw \$6, 20(\$7); add \$8, \$6, \$3; or \$1, \$6, \$6; add \$8, \$3, \$2; sw \$8, 20(\$1). Identify and explain the hazards in the code sequence and how they are resolved. Specify how many clock cycles does it take to execute the code sequence in the two configurations.

1. lw \$6, 20(\$7); $RF[\$6] \leftarrow M[RF[\$7] + 20]$
2. add \$8, \$6, \$3; $RF[\$8] \leftarrow RF[\$6] + RF[\$3]$
3. or \$1, \$6, \$6; $RF[\$1] \leftarrow RF[\$6] + RF[\$6]$
4. add \$8, \$3, \$2; $RF[\$8] \leftarrow RF[\$3] + RF[\$2]$
5. sw, 20(\$1) $M[RF[\$1] + 20] \leftarrow RF[\$8]$

RAW: Instr 2 with Instr 1 → \$6

resolved by forwarding from Mem stage of Instr1 to EX stage of Instr2 + 1 stall

RAW: Instr 3 with Instr 1 → \$6

No longer a hazard – WB for \$6 in first half of clk cycle 5, read in ID in second half of clk cycle 5


RAW: Instr 5 with Instr 3 → \$1

Resolved by forwarding from M stage of Instr 3 to EX stage of Instr 5

RAW: Instr 5 with Instr 2, 4 → \$8

Resolved by forwarding from M stage of Instr 4 to M stage of Instr 5

10 clock cycles to execute

 

Pipeline diagram with forwarding